

Smart Adaptive Traffic Light Controller

Prepared by: Lavanya Tamgade


Introduction

Modern cities face heavy traffic congestion that requires intelligent management systems. Conventional traffic light controllers use fixed-time schedules, which may not be efficient under varying traffic conditions. This project implements a Smart Adaptive Traffic Light Controller using Verilog HDL. The controller dynamically adjusts the green light duration based on traffic density inputs from each direction, ensuring optimal flow and reducing waiting times. The design is implemented as a Moore FSM with adaptive timing logic.


Key Highlights

- Objective: Design and simulate an adaptive traffic light controller in Verilog.
- FSM States: NS_GREEN, NS_YELLOW, ALL_RED_1, EW_GREEN, EW_YELLOW, ALL_RED_2.
- Key Parameters: BASE_GREEN=6, DENSITY_STEP=4, YELLOW_TIME=3, ALL_RED_TIME=2.
- Adaptive Feature: Green time = BASE_GREEN + (DENSITY_STEP × density_input).
- Safety: Mutual exclusion of greens; yellow & all-red intervals enforced.

FSM State Diagram

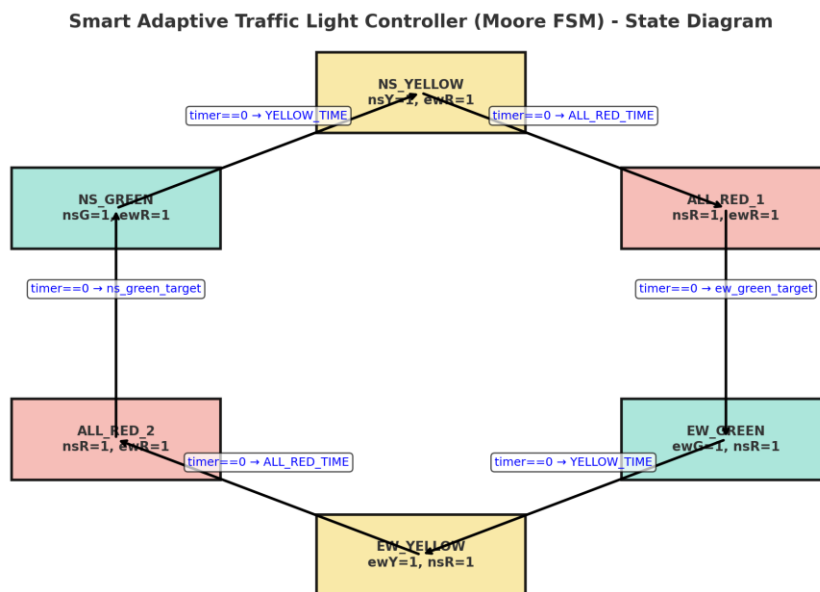

 
Timing (One Full Cycle with Adaptive Green)



Parameters & Adaptation

Green targets are computed as: $\text{BASE_GREEN} + \text{DENSITY_STEP} \times \text{density}$. Example: For NS density=2 and EW density=0, the green targets become NS=14 and EW=6 cycles. Yellow time is fixed at 3 cycles, while all-red intervals last 2 cycles to ensure safety.

Synthesized Schematic (High-level)

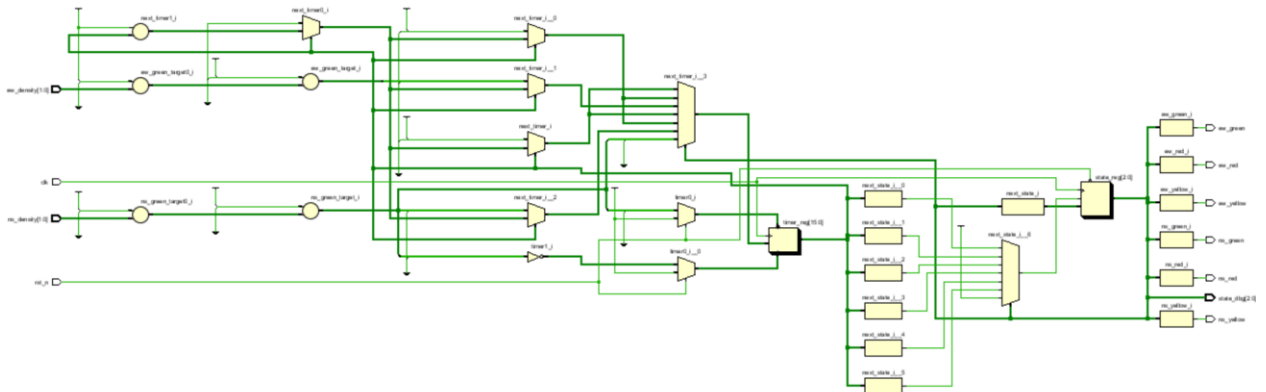

Appendix A — Verilog RTL

```
`timescale 1ns / 1ps

// -----

// Smart Adaptive Traffic Light Controller (NS <-> EW)

// - Adaptive GREEN time based on 2-bit density inputs

// - Simple 5-state FSM: NS_G, NS_Y, ALL_RED1, EW_G, EW_Y, ALL_RED2

// - Timing is in "clock cycles" for easy simulation

// -----

module smart_traffic_controller #(

    parameter integer BASE_GREEN  = 6, // base green duration

    parameter integer DENSITY_STEP = 4, // extra cycles per density level

    parameter integer YELLOW_TIME  = 3, // yellow duration

    parameter integer ALL_RED_TIME = 2  // all-red safety duration

)(

    input wire    clk,

    input wire    rst_n,    // active-low reset

    input wire [1:0] ns_density,    // 00=low, 01=med, 10=high, 11=very high

    input wire [1:0] ew_density,    // same encoding for EW

    output reg     ns_red,

    output reg     ns_yellow,

    output reg     ns_green,

    output reg     ew_red,

    output reg     ew_yellow,

    output reg     ew_green,
```

```

        output reg [2:0] state_dbg    // for waveform/debug
    );

    // FSM states

    localparam [2:0]

        S_NS_GREEN = 3'd0,

        S_NS_YELLOW = 3'd1,

        S_ALL_RED_1 = 3'd2,

        S_EW_GREEN = 3'd3,

        S_EW_YELLOW = 3'd4,

        S_ALL_RED_2 = 3'd5;

    reg [2:0] state, next_state;

    reg [15:0] timer, next_timer;

    // computed green targets

    wire [15:0] ns_green_target = BASE_GREEN + DENSITY_STEP * ns_density;

    wire [15:0] ew_green_target = BASE_GREEN + DENSITY_STEP * ew_density;

    // timer tick + state register

    always @(posedge clk or negedge rst_n) begin

        if (!rst_n) begin

            state <= S_NS_GREEN;

            timer <= ns_green_target;

```

```

    end else begin

        state <= next_state;

        timer <= next_timer;

    end

end

// next-state & timer logic

always @* begin

    // default hold

    next_state = state;

    next_timer = (timer == 0) ? 0 : (timer - 1);

case (state)

    S_NS_GREEN: begin

        if (timer == 0) begin

            next_state = S_NS_YELLOW;

            next_timer = YELLOW_TIME;

        end

    end

    S_NS_YELLOW: begin

        if (timer == 0) begin

            next_state = S_ALL_RED_1;

            next_timer = ALL_RED_TIME;

        end

    end

```

```
end

S_ALL_RED_1: begin

    if (timer == 0) begin

        next_state = S_EW_GREEN;

        next_timer = ew_green_target;

    end

end

S_EW_GREEN: begin

    if (timer == 0) begin

        next_state = S_EW_YELLOW;

        next_timer = YELLOW_TIME;

    end

end

S_EW_YELLOW: begin

    if (timer == 0) begin

        next_state = S_ALL_RED_2;

        next_timer = ALL_RED_TIME;

    end

end

S_ALL_RED_2: begin

    if (timer == 0) begin

        next_state = S_NS_GREEN;

        next_timer = ns_green_target;

    end

end
```

```

    end

    default: begin

        next_state = S_NS_GREEN;

        next_timer = ns_green_target;

    end

endcase

end

// outputs (Moore)

always @* begin

    // defaults

    ns_red   = 1'b0; ns_yellow = 1'b0; ns_green = 1'b0;

    ew_red   = 1'b0; ew_yellow = 1'b0; ew_green = 1'b0;

    case (state)

        S_NS_GREEN: begin ns_green = 1'b1; ew_red = 1'b1; end

        S_NS_YELLOW: begin ns_yellow = 1'b1; ew_red = 1'b1; end

        S_ALL_RED_1: begin ns_red = 1'b1; ew_red = 1'b1; end

        S_EW_GREEN: begin ew_green = 1'b1; ns_red = 1'b1; end

        S_EW_YELLOW: begin ew_yellow = 1'b1; ns_red = 1'b1; end

        S_ALL_RED_2: begin ns_red = 1'b1; ew_red = 1'b1; end

        default: begin ns_red = 1'b1; ew_red = 1'b1; end

    endcase

end

```

```
// expose state for debug

always @* state_dbg = state;

endmodule
```

Appendix B — Testbench

```
`timescale 1ns/1ps

module tb_smart_traffic_controller;

    reg clk;

    reg rst_n;

    reg [1:0] ns_density;

    reg [1:0] ew_density;

    wire ns_red, ns_yellow, ns_green;

    wire ew_red, ew_yellow, ew_green;

    wire [2:0] state_dbg;

    // DUT

    smart_traffic_controller #(

        .BASE_GREEN (6),
```



```
.DENSITY_STEP(4),  
  
.YELLOW_TIME (3),  
  
.ALL_RED_TIME(2)  
  
) dut (  
  
.clk(clk),  
  
.rst_n(rst_n),  
  
.ns_density(ns_density),  
  
.ew_density(ew_density),  
  
.ns_red(ns_red),  
  
.ns_yellow(ns_yellow),  
  
.ns_green(ns_green),  
  
.ew_red(ew_red),  
  
.ew_yellow(ew_yellow),  
  
.ew_green(ew_green),  
  
.state_dbg(state_dbg)  
  
);
```

```
// 100 MHz clock
```

```
initial clk = 1'b0;
```

```
always #5 clk = ~clk;
```

```
// Simple progress print (no %s)
```

```
always @(posedge clk) begin
```

```
$display("t=%0t ns / state=%0d / NS(RYG)=%0d%0d%0d  
EW(RYG)=%0d%0d%0d / dens NS=%0d EW=%0d",
```

```
$time,
```

```
state_dbg,
```

```
ns_red, ns_yellow, ns_green,
```

```
ew_red, ew_yellow, ew_green,
```

```
ns_density, ew_density
```

```
);
```

```
end
```

```
// Assertions (keep them)
```

```
always @(posedge clk) begin
```

```
if (rst_n) begin
```

```
if (ns_green && ew_green) begin
```

```
$display("ASSERT FAIL @%0t: Both directions GREEN!", $time);
```

```
$fatal;
```

```
end
```

```
if (ns_yellow && ew_yellow) begin
```

```
$display("ASSERT FAIL @%0t: Both directions YELLOW!", $time);
```

```
$fatal;
```

```
end
```

```
end
```

```
end
```

```

// Stimulus

initial begin

    // Ensure known values before first time step

    rst_n    = 1'b0;

    ns_density = 2'd2; // NS high

    ew_density = 2'd0; // EW low


    // Startup banner (helps spot if TB is actually running)

    $display("TB start @ %0t", $time);


    repeat (3) @(posedge clk);

    rst_n = 1'b1;


    repeat (40) @(posedge clk);


    $display("\n-- Changing densities: NS low, EW very high --\n");

    ns_density = 2'd0;

    ew_density = 2'd3;

    repeat (50) @(posedge clk);


    $display("\n-- Changing densities: both medium --\n");

    ns_density = 2'd1;

    ew_density = 2'd1;

    repeat (40) @(posedge clk);

```

```
$display("\nSimulation finished OK.");
```

```
$finish;
```

```
end
```

```
endmodule
```

Conclusion

Simulation and analysis confirm that the Smart Adaptive Traffic Light Controller meets its objectives. The FSM transitions are correct, mutual exclusion of green signals is maintained, and adaptive timing based on density inputs is verified. This design can be synthesized on FPGA and extended with real sensor inputs for real-world deployment.